

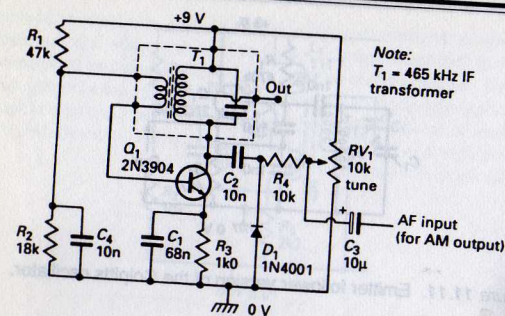


Figure 11.13. 465kHz B.F.O. with varactor tuning and FM facility.

Figure 11.14 shows a wide-range crystal oscillator designed for use with a parallel-mode crystal. This is actually a Pierce oscillator circuit, and can be used with virtually any good 100kHz to 5MHz parallel-mode crystal without need for circuit modification.

Alternatively, Figure 11.15 shows a 100kHz Colpitts oscillator designed for use with a series-mode crystal. Note that the L_1 - C_1 - C_2 tuned circuit is designed to resonate at the same frequency as the crystal, and that its component values must be changed if other crystal frequencies are used.

Finally, Figure 11.16 shows an exceptionally useful two-transistor oscillator that can be used with any 50kHz to 10MHz series-resonant crystal. Q_1 is wired as a common-base amplifier and Q_2 is an emitter follower, and the output signal (from Q_2 emitter) is fed back to the input (Q_1 emitter) via C_2 and the series-resonant crystal. This excellent circuit will oscillate with any crystal that shows the slightest sign of life.

White noise generator

One useful 'linear' but non-sinusoidal waveform is that known as 'white noise', which contains a full spectrum of randomly generated frequencies, each with equal mean power when averaged over a unit of

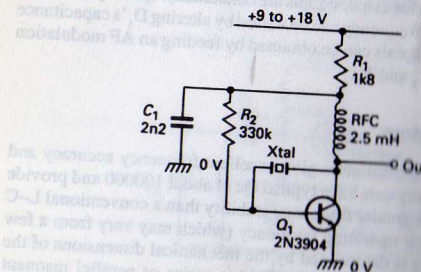


Figure 11.14. Wide-range Pierce oscillator uses parallel mode crystal.

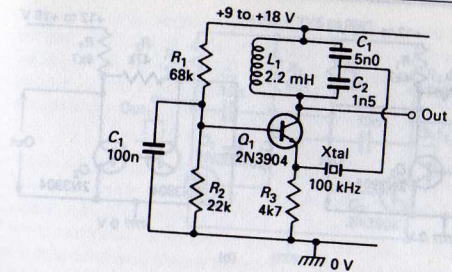


Figure 11.15. 100kHz Colpitts oscillator uses series-mode crystal.

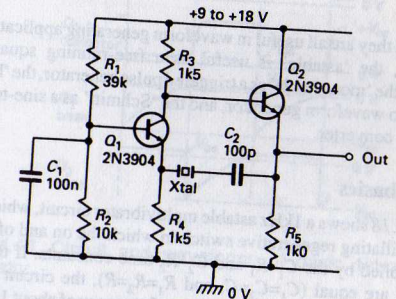


Figure 11.16. Wide-range (50kHz-10MHz oscillator can be used with almost any series-mode crystal.

time. White noise is of value in testing AF and RF amplifiers, and is widely used in special-effects sound generator systems.

Figure 11.17(a) shows a simple white noise generator that relies on the fact that all Zener diodes generate substantial white noise when operated at a low current. R_2 and ZD₁ are wired in a negative-feedback loop between the collector and base of common-emitter amplifier Q_1 , thus stabilising the circuits d.c. working levels, and the loop is a.c.-decoupled via C_1 . ZD₁ thus acts as a white noise source that is wired in series with the base of Q_1 , which amplifies the noise to a useful level of about 1V0 peak-to-peak. Any 5V6 to 12V Zener diode can be used in this circuit.

Figure 11.17(b) is a simple variation of the above design, with the reverse-biased base-emitter junction of a 2N3904 transistor (which 'generates' at about 6V) used as the noise-generating Zener diode.

Multivibrator circuits

Multivibrators are two-state circuits that can be switched between one state and the other via a suitable trigger signal, which may be generated either internally or externally. There are four basic types of 'multi'