


PART 1

THE 2SK77B SINGLE-ENDED AMPLIFIER


YAMAHA B1




2SK77 CURVE

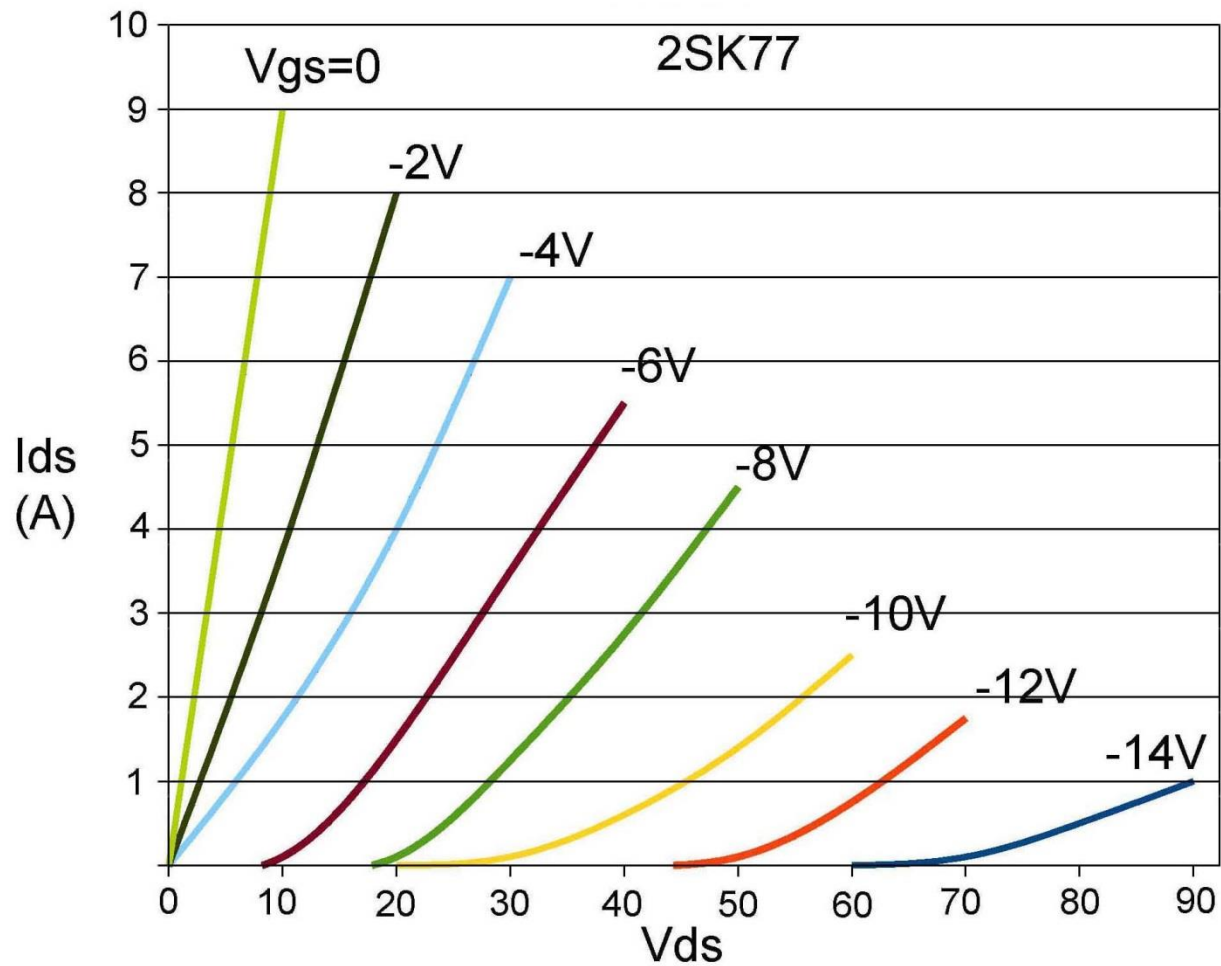

YAMAHA B1 SIMPLIFIED

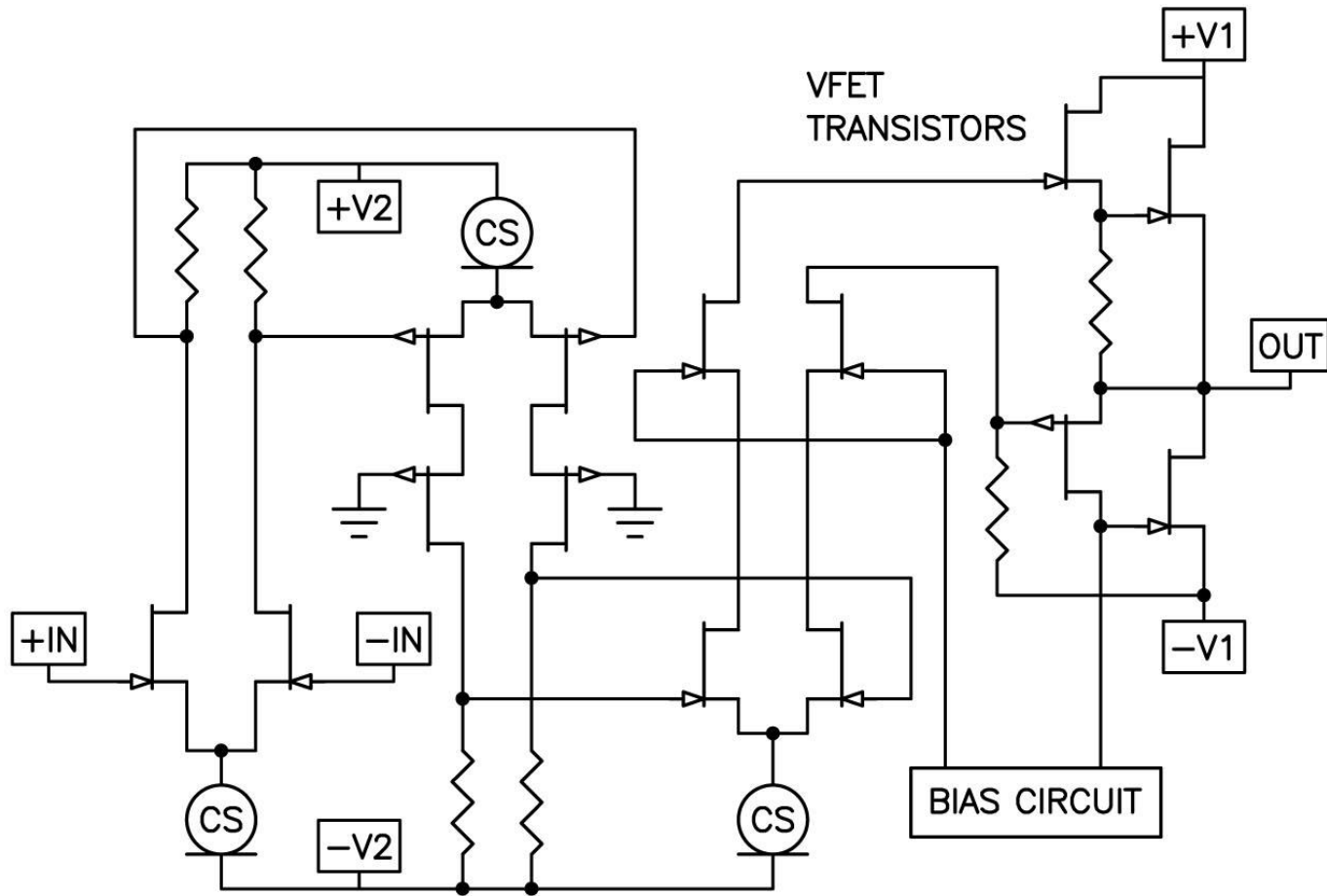


YAMAHA B1 FULL

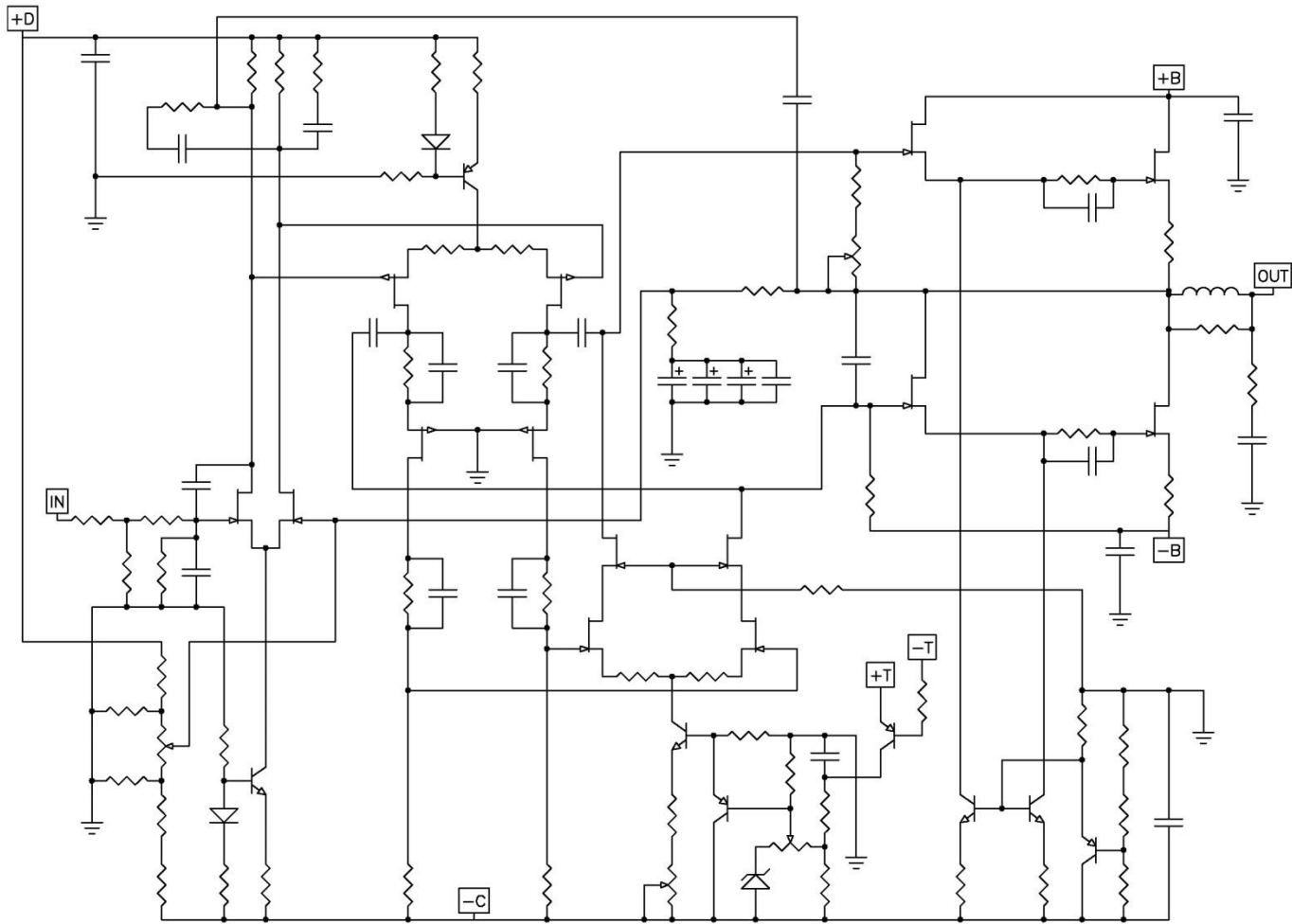


2SK77B




2SK77B CURVE

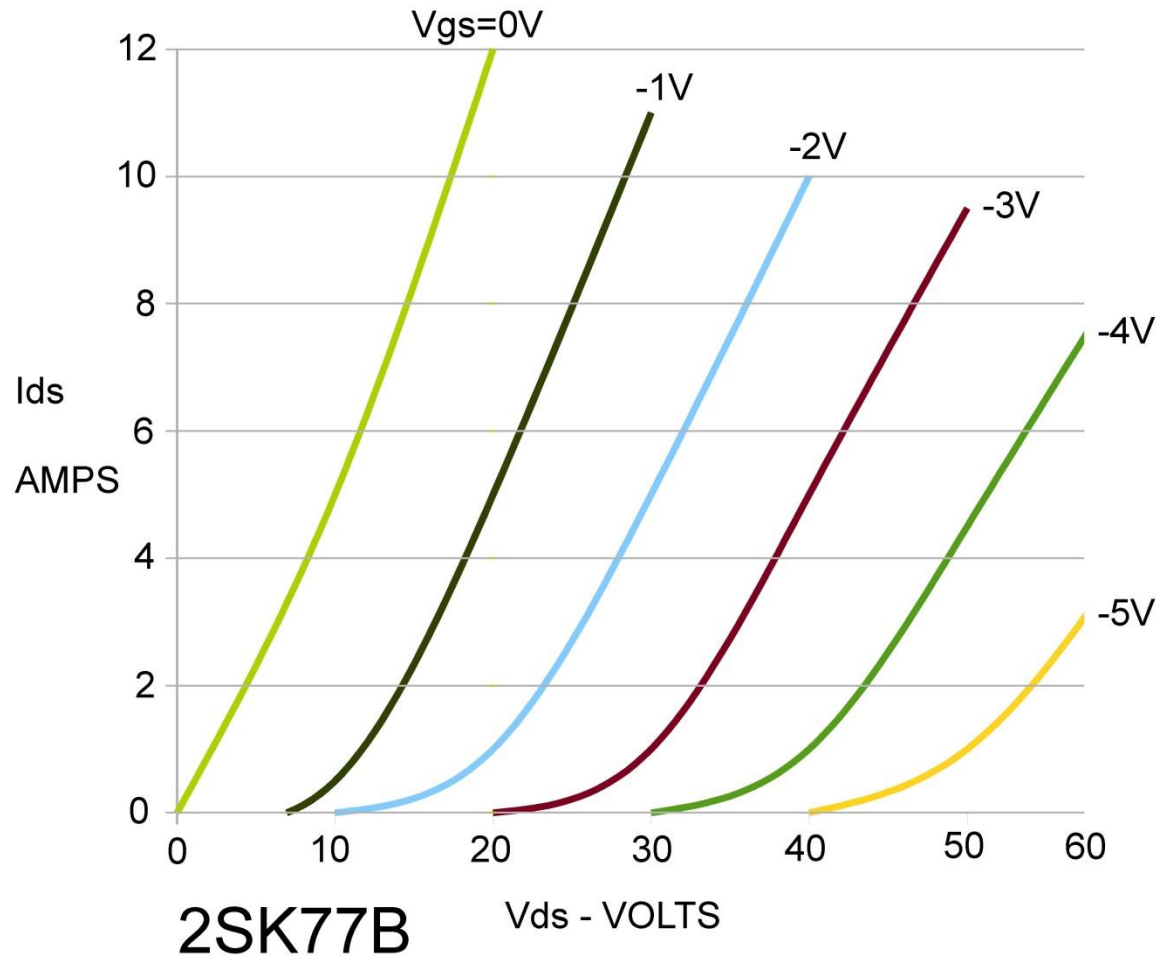


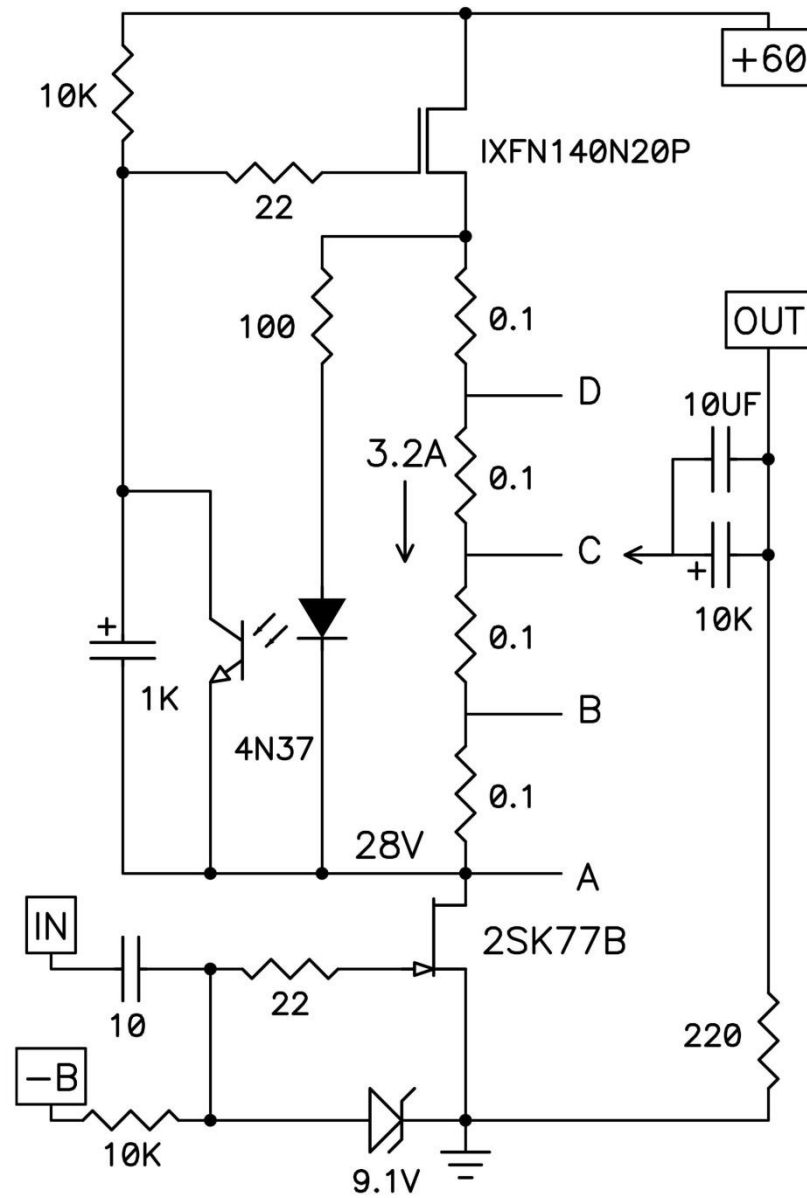


2SK77B 50 WATT VFET AMPLIFIER

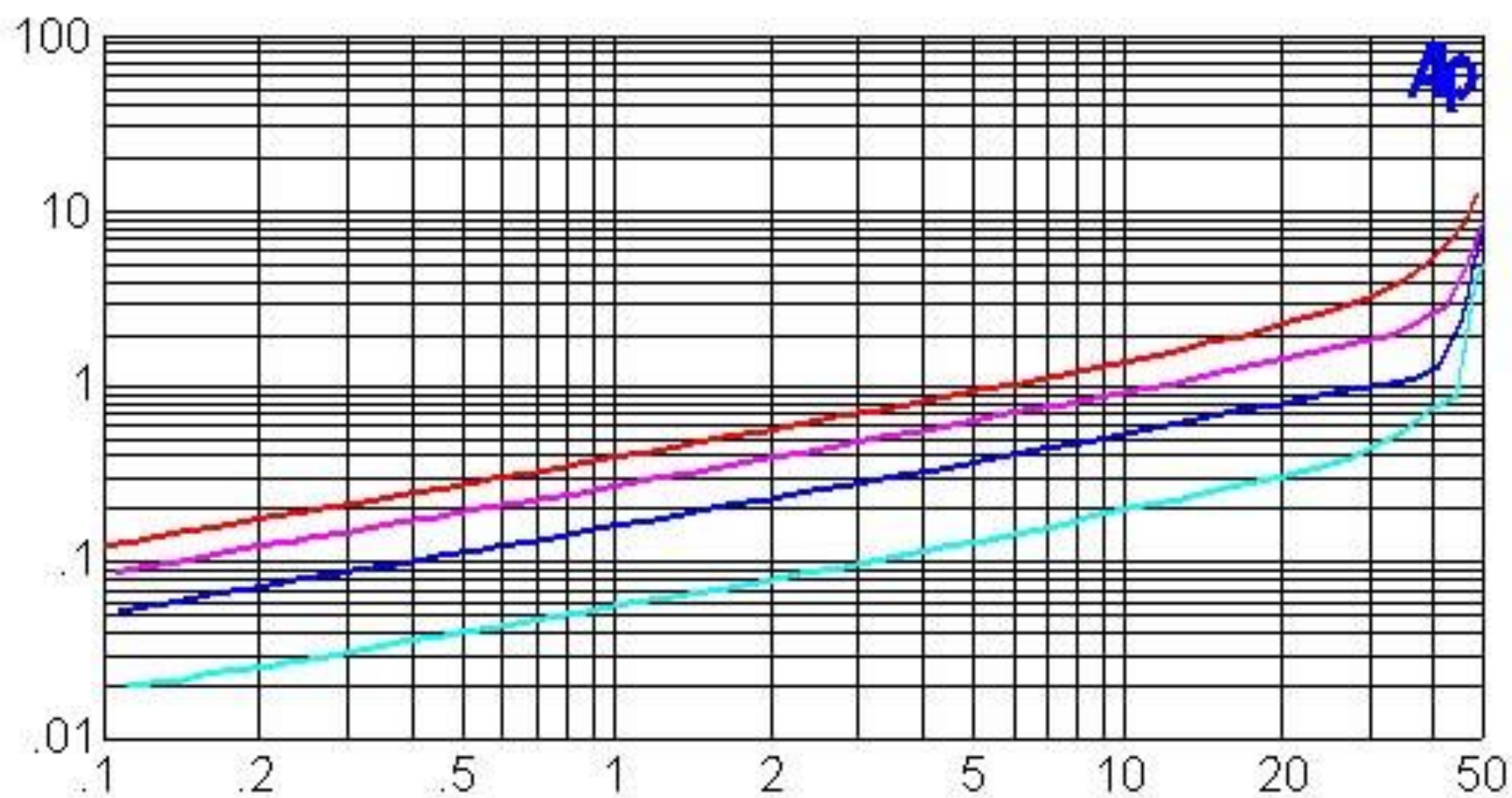

2SK77B AMPLIFIER - DISTORTION VS POWER

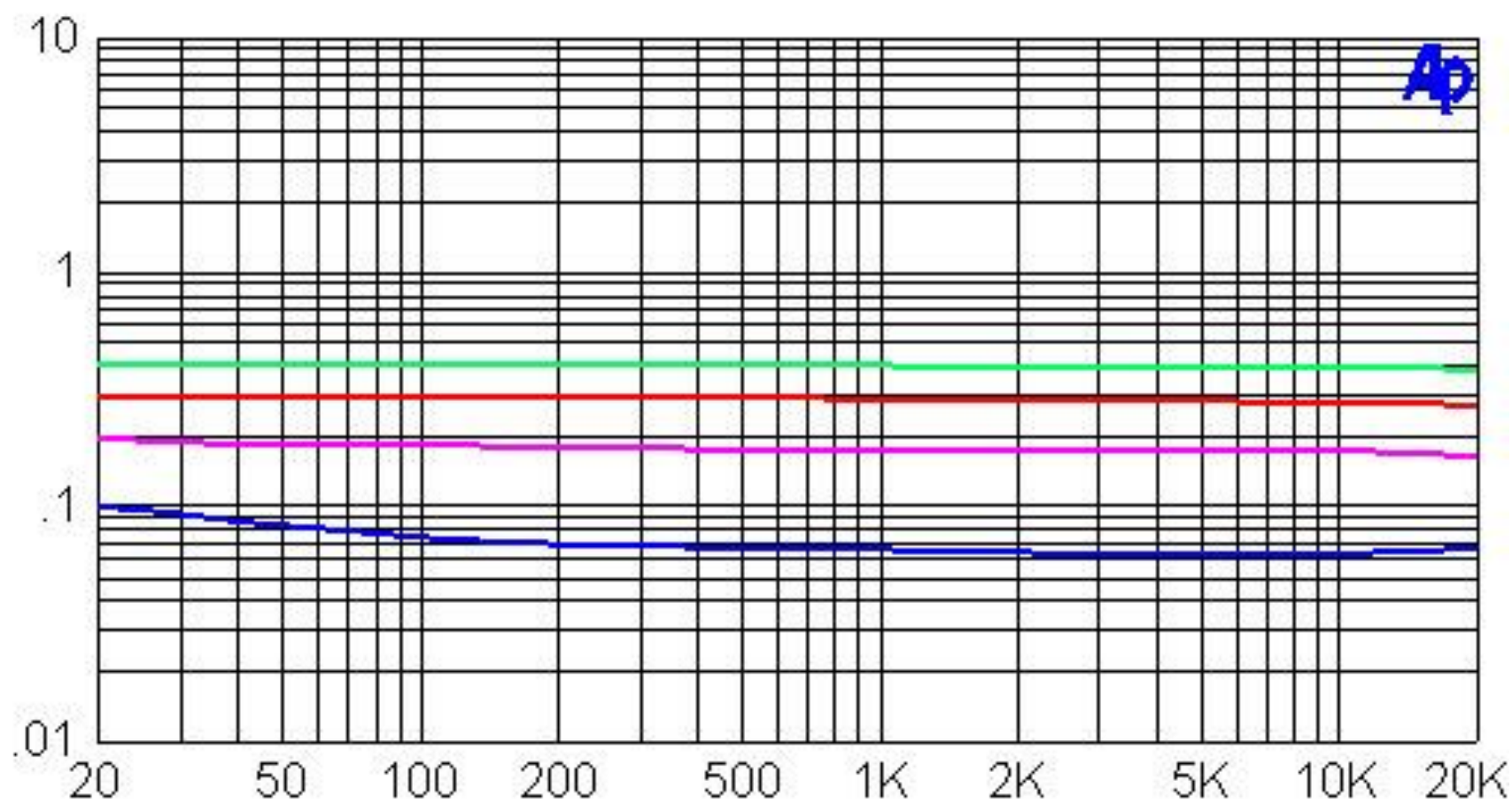

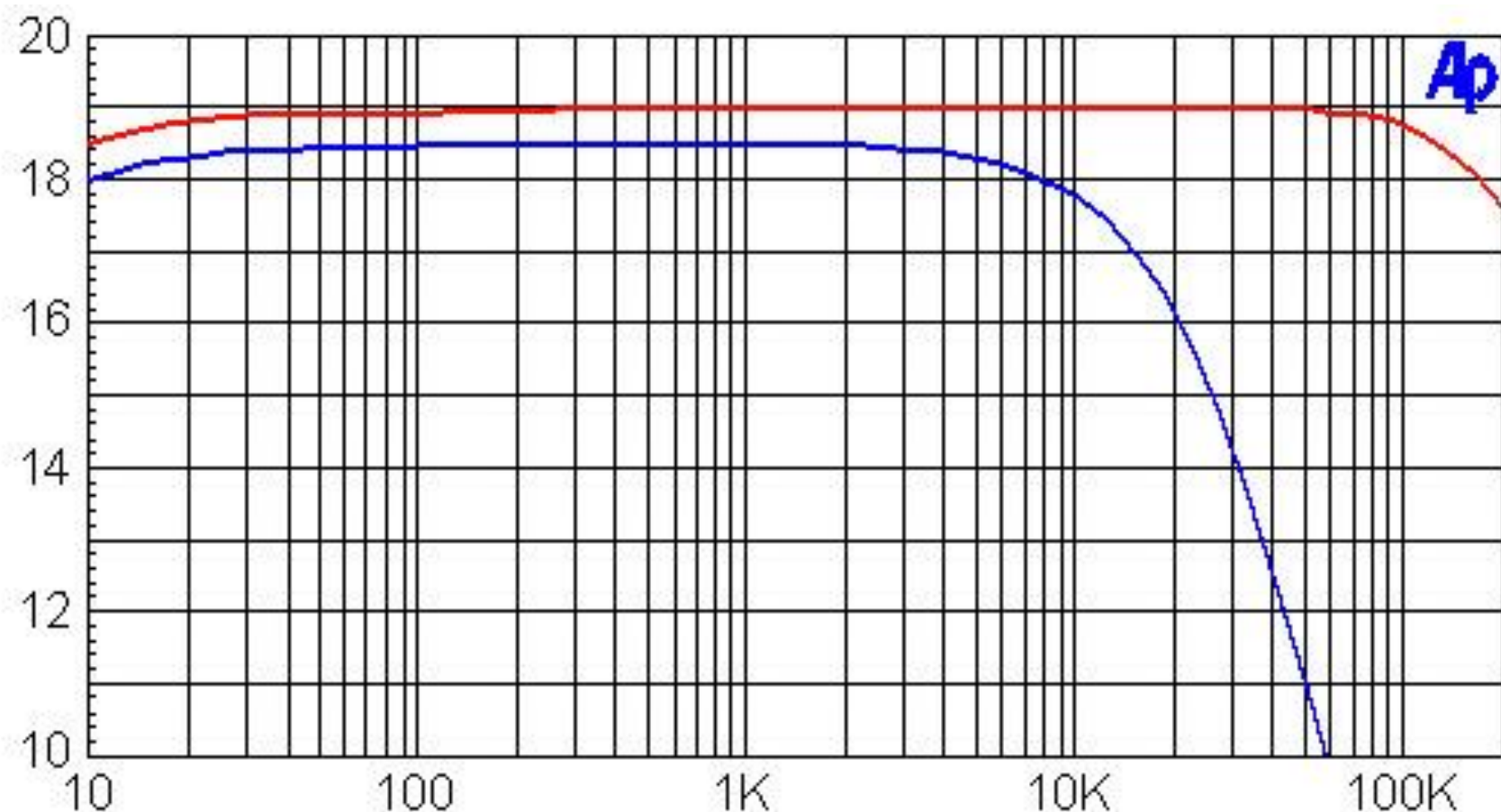2SK7B AMPLIFIER - DISTORTION VS FREQUENCY




2SK77B AMPLIFIER - FREQUENCY RESPONSE
DB VS FREQ 25 OHM / 600 OHM SOURCE

PART 2


IXFN140N20P

SINGLE-ENDED AMP

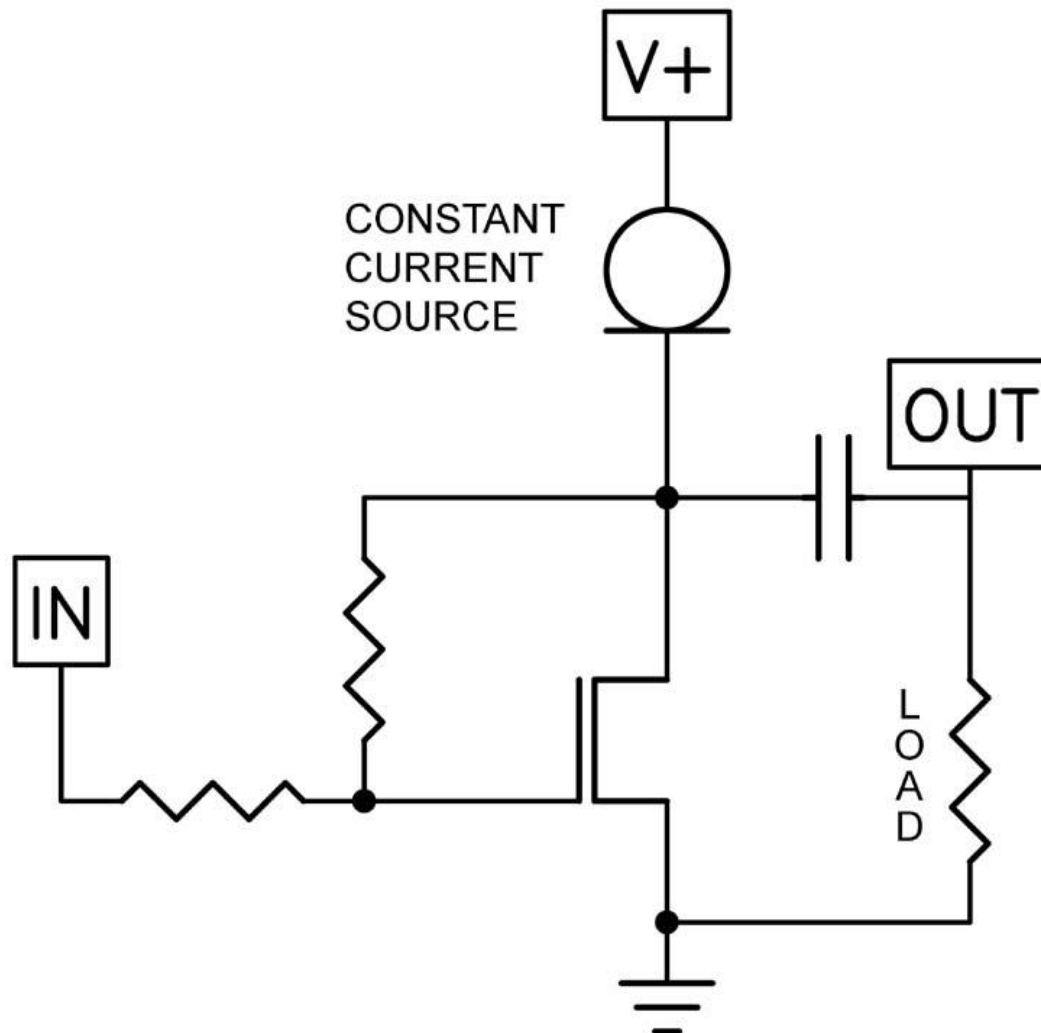


SCHADE FEEDBACK

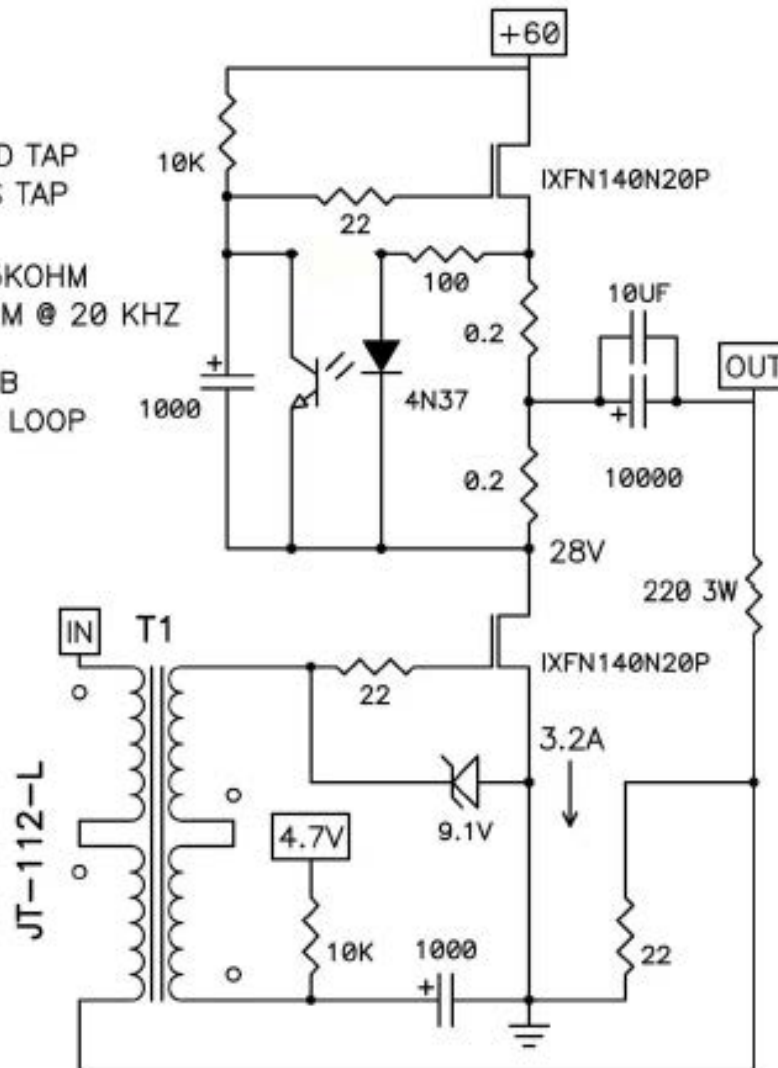
NOTES
 DF=12.5 MID TAP
 DF=7.3 CCS TAP
 INPUT Z = 5KOHM
 AND 600 OHM @ 20 KHZ
 GAIN = 20 dB
 38 dB OPEN LOOP




MOSFET AMPLIFIER WITH IXFN140N20P

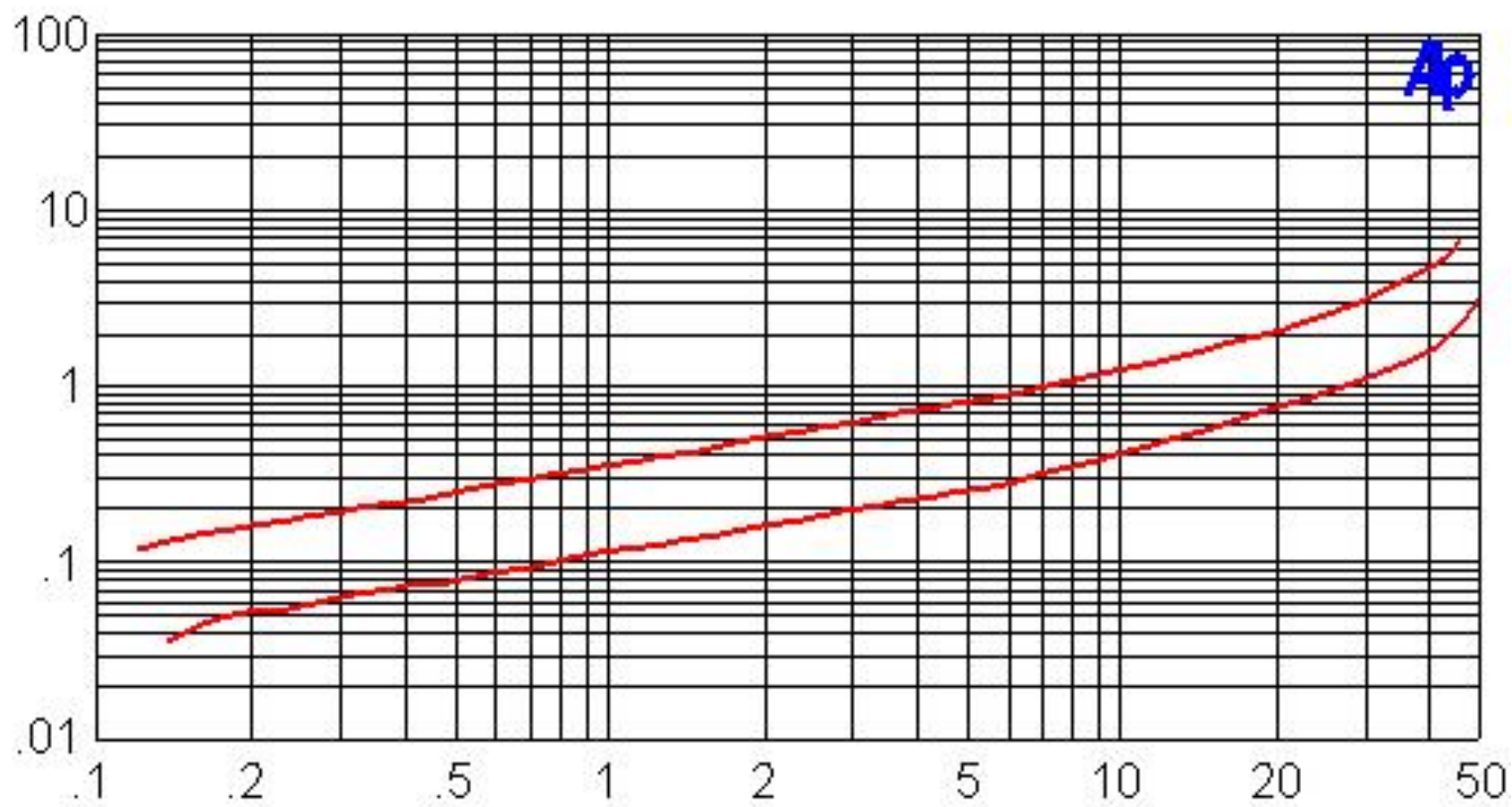

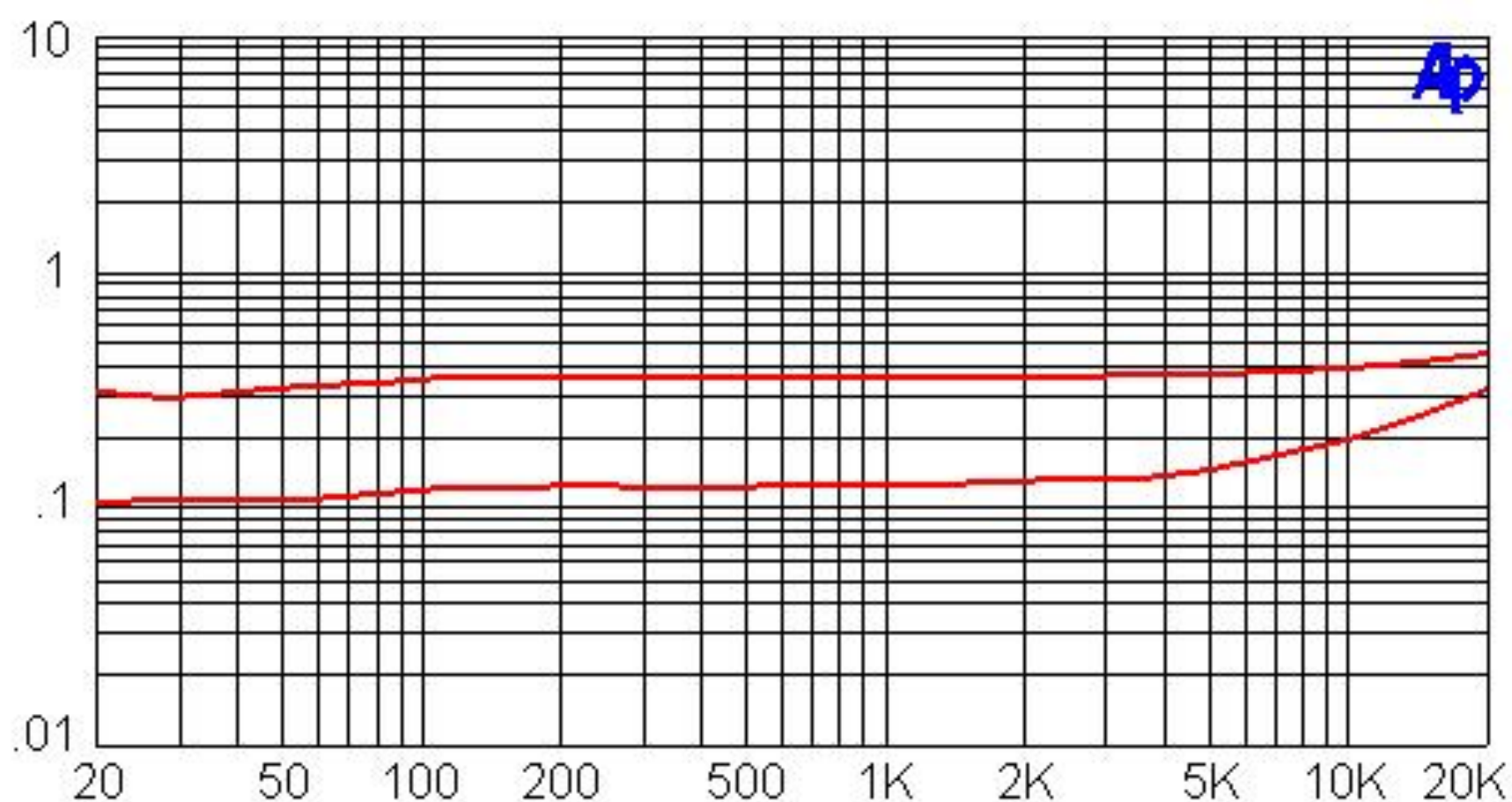IXFN140N20P AMPLIFIER - DISTORTION VS POWER
8 OHMS 1 KHZ CCS VS MIDDLE TAP



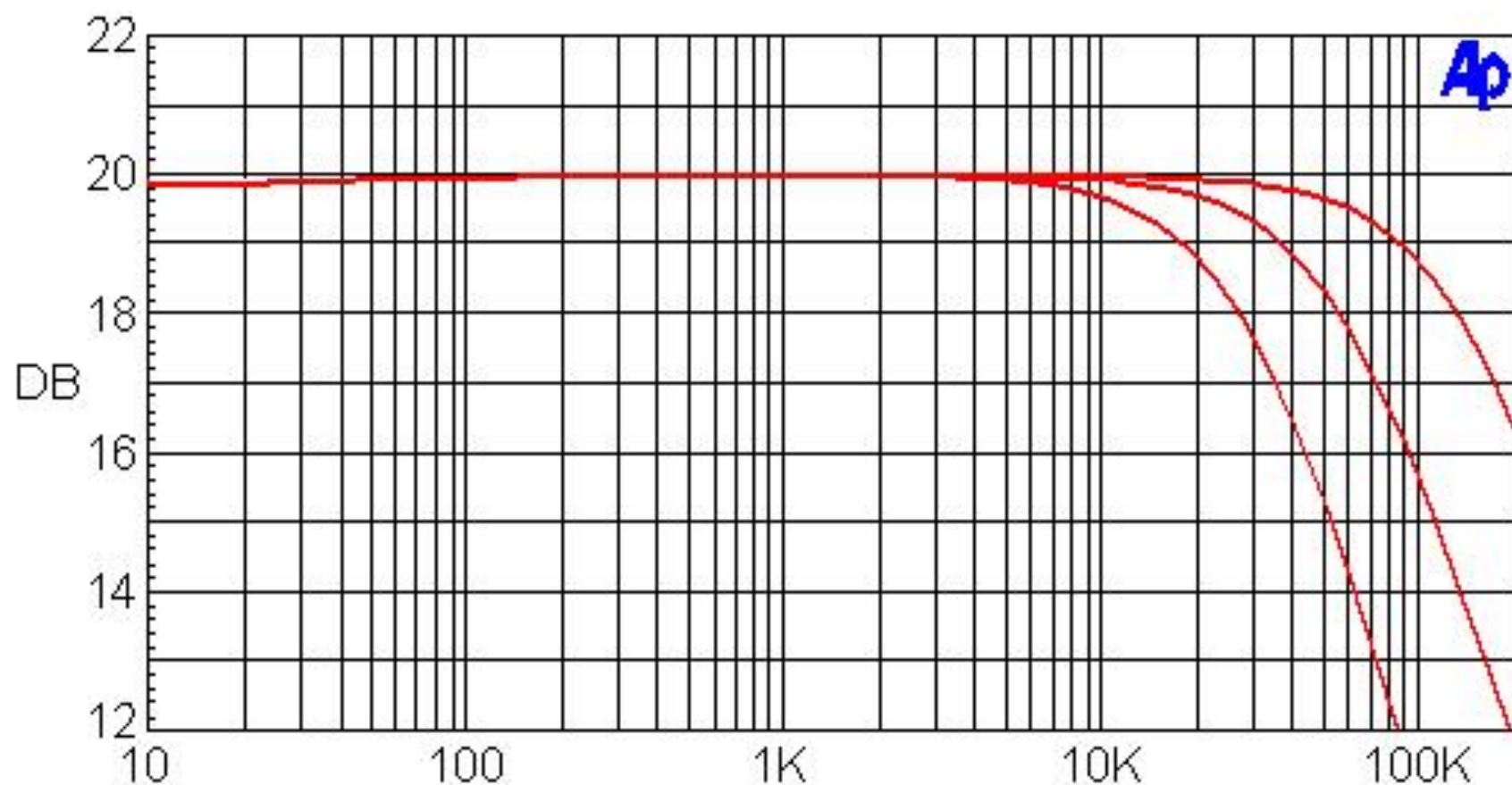INFN140N20P AMPLIFIER - DISTORTION VS FREQ
1W 8 OHM CCS AND MIDDLE TAP




IXSYS IXFN140N20P AMPLIFIER - FREQ RESPONSE
1W 8 OHM MIDDLE TAP 50, 100, 200 OHM SOURCE


PART 3

SAL FULL RANGE
LOUDSPEAKER




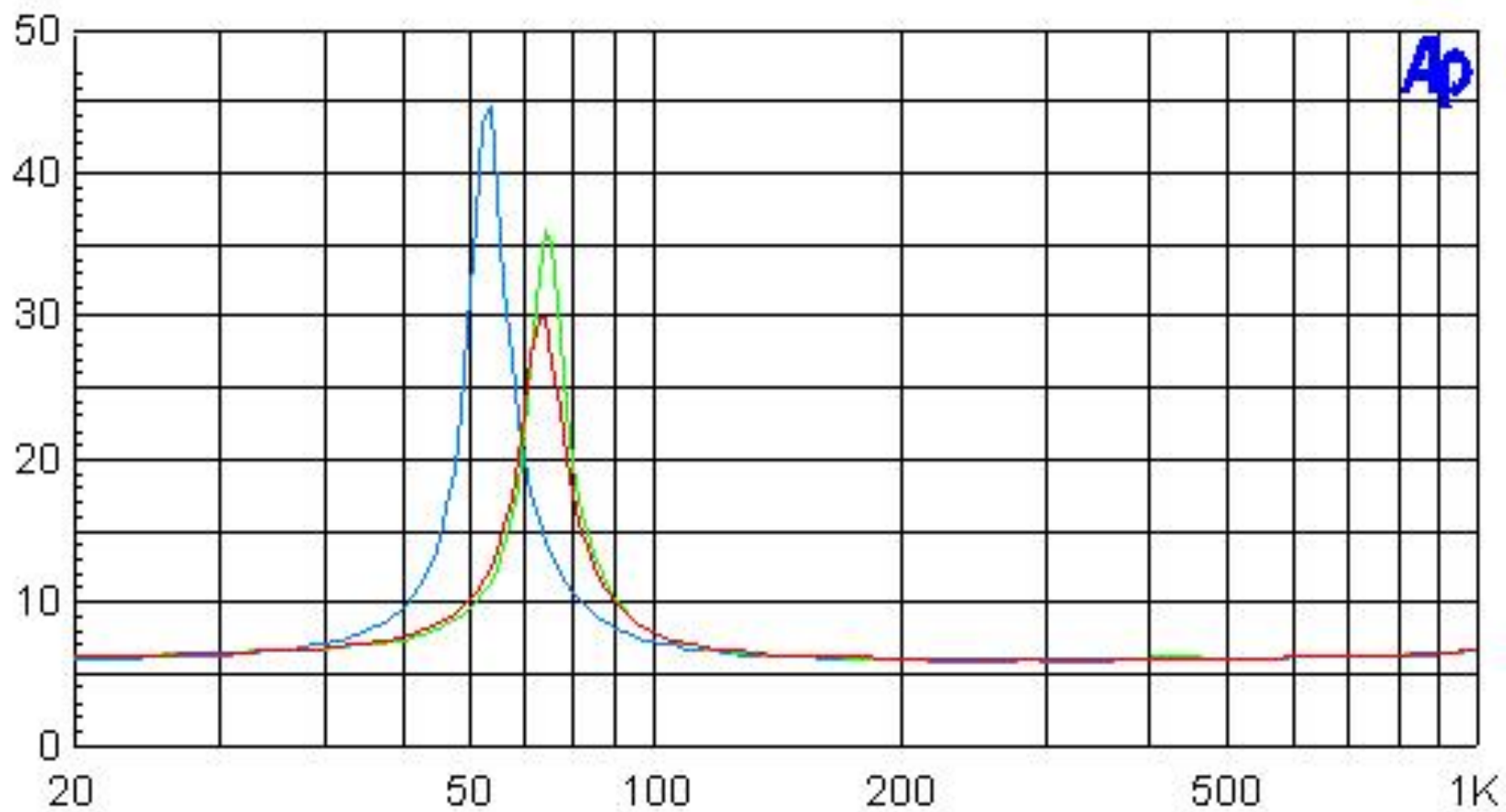

SAL DRIVER IMPEDANCE VS FREQUENCY

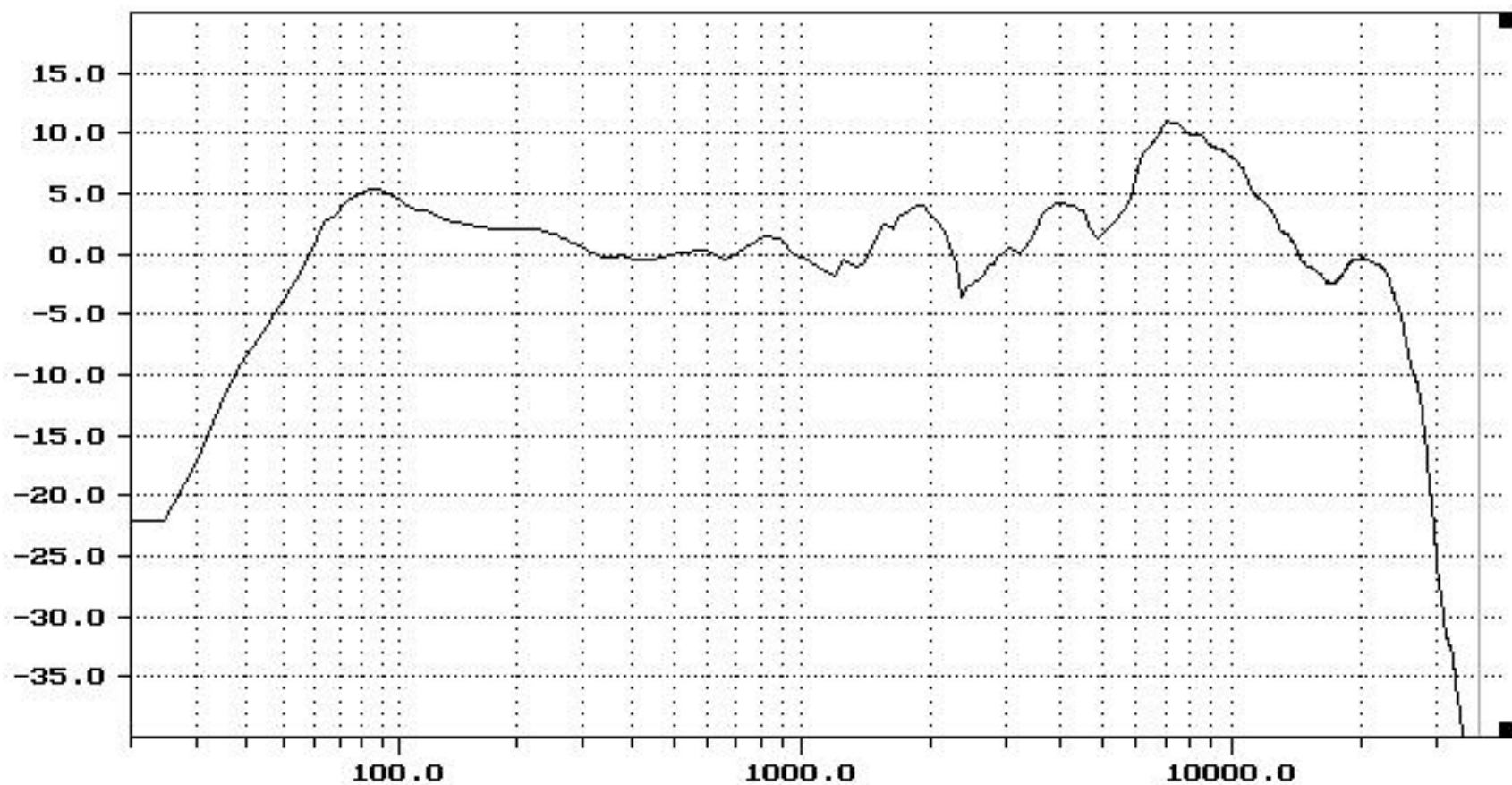

SAL RESPONSE @ 1M / NF (400HZ)

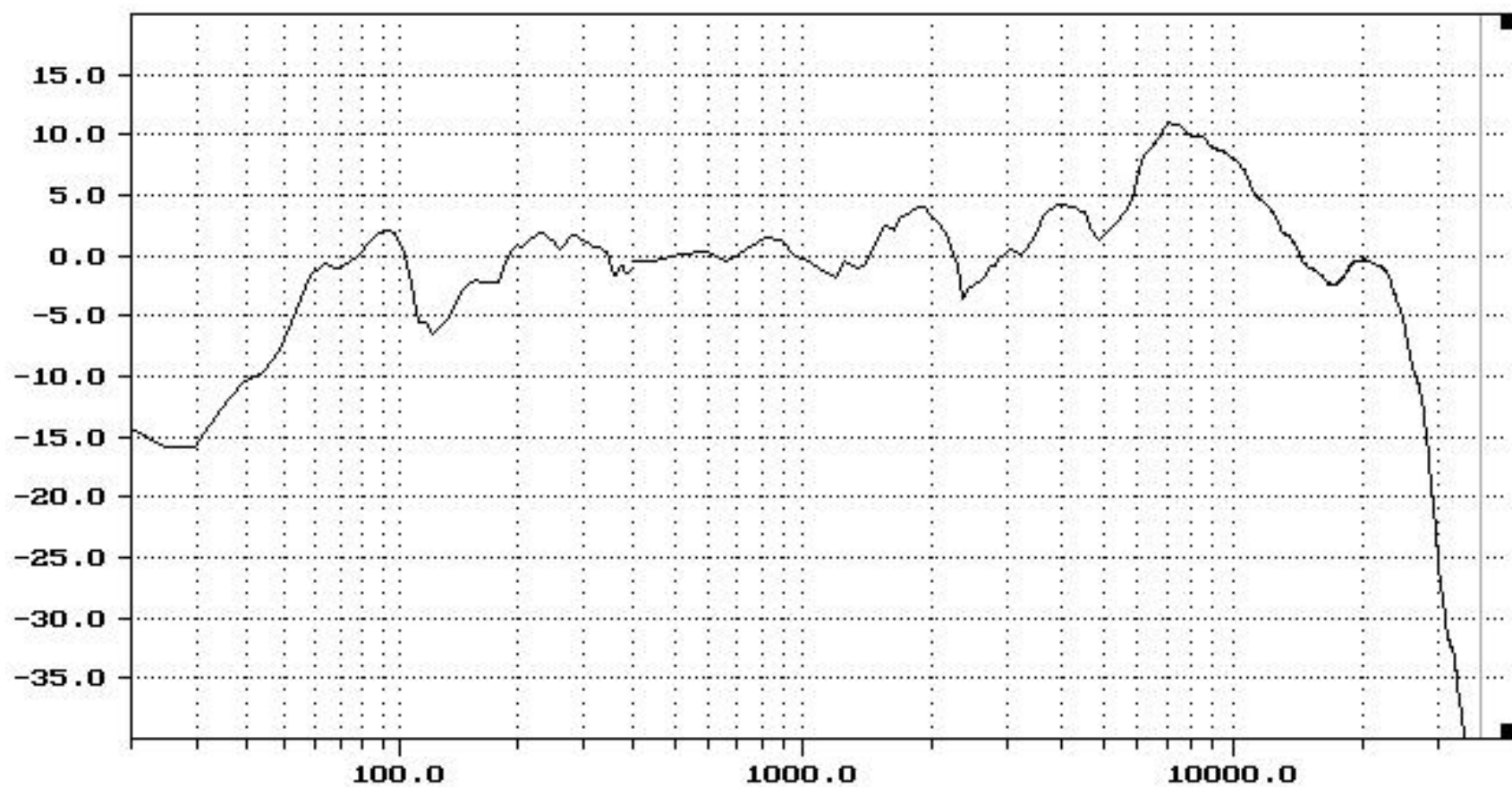

SAL RESPONSE @ 1M

