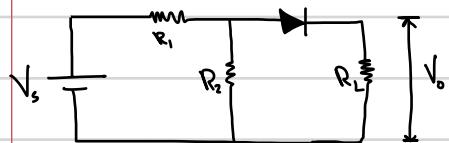


Study - 1) In the circuit shown below, the Si diode is a practical device biased for forward conduction. $R_1 = 1\text{ k}\Omega$; $R_2 = 5\text{ k}\Omega$ and $V_s = 10\text{ V}$. At room temperature, the diode exhibits a reverse saturation current (I_s) of $1.5\text{ }\mu\text{A}$. What is the load resistance R_L ?

Calculate the Ratio of power dissipated in the diode and the power dissipated in the load (R_L). Express your answer in dB.



$$R_1 = 1\text{ k}\Omega$$

$$R_2 = 5\text{ k}\Omega$$

$$V_s = 10\text{ V}$$


$$I_s = 1.5\text{ }\mu\text{A}$$

$$R_L = ?$$

$$P_D = P_L$$

$$V_o = \left(\frac{R_2}{R_1 + R_2} \right) V_s = \left(\frac{5\text{ k}\Omega}{1\text{ k}\Omega + 5\text{ k}\Omega} \right) 10\text{ V} = 8.33\text{ V}$$
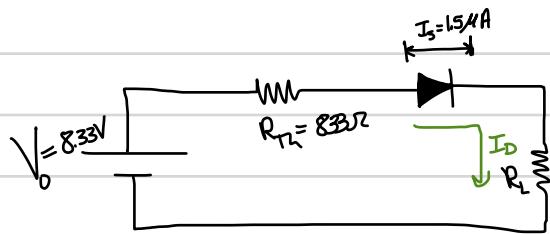
$$R_1 \parallel R_2 = \frac{1}{\frac{1}{5\text{ k}\Omega} + \frac{1}{1\text{ k}\Omega}} = 833\text{ }\Omega$$



$$I_D = I_s e^{\frac{V_o}{0.026}} = 1.5\text{ }\mu\text{A} e^{\frac{8.33\text{ V}}{0.026}} =$$

$$R_L = \frac{V_o}{I_D} =$$