

Figure 1 This simple current sink allows you to test both the static and the dynamic behavior of power supplies.