

10 kHz SQUARE WAVE
OSCILLATOR


BANDPASS FILTER
GAIN = 0.5 Q = 5
BW = 2kHz

2 & 4 WIRE
CONNECTIONS
TWO WIRE USE: TP1 &
TP2

DIFF. AMP
GAIN x33

SYNCHRONOUS
DETECTOR
GAIN +/- 1

LOW PASS FILTER
& 2V DIGITAL PANEL
METER

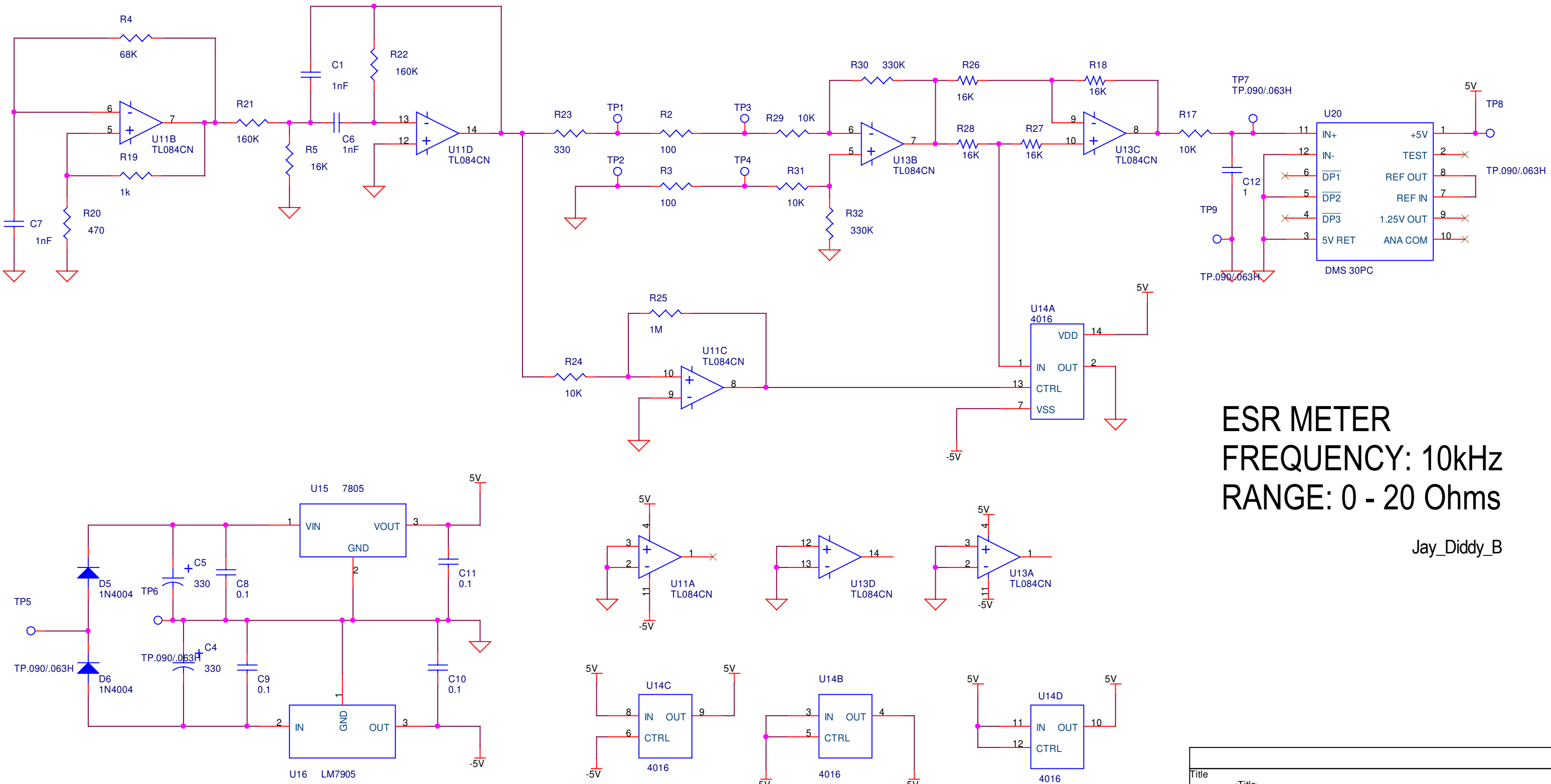

ESR METER
FREQUENCY: 10kHz
RANGE: 0 - 20 Ohms

Jay_Diddy_B

Title <Title>		
Size B	Document Number <Doc>	Rev <RevCode>
Date:	Sunday, November 10, 2013	Sheet 1 of 1